



(15')
Abonus.

$$\bar{U}_{Lc} \Rightarrow \bar{U}_{ab} = \bar{U}_{an} \cdot (\sqrt{3} \angle 30^\circ) = 374,809 \cdot \sqrt{24,5157} \angle -5,484^\circ \text{ V}$$

$$\bar{U}_{an} = \frac{240 \angle 0^\circ}{0,15 + j2,63 + 15 + j10} \cdot (15 + j10) = 215,41 - j20,682 = 216,3961 \angle -5,484^\circ \text{ V}$$

$$\bar{I}_a = 9,3054 - j7,5824 = 12,0035 \angle -39,1744^\circ \text{ A}$$

b) \dot{w} ? $w \cdot \sqrt{3} = Q_T$

$$w = \frac{Q}{\sqrt{3}} = \frac{(I_a^2 \cdot j10) \cdot 3}{\sqrt{3}} \cdot \sqrt{3} (I_a^2 \cdot j10) = 2495,60829 \text{ W}$$

c) $P_T = I_a^2 \cdot R \cdot 3 = 6483,78 \text{ W}$ $\tan \varphi = \frac{Q_T}{P_T} \Rightarrow 33,69 = \varphi \Rightarrow \tan \varphi = 0,6666$
 $Q_T = 3 \cdot I_a^2 \cdot X_L = 4322,52 \text{ VAR}$

$$Q_c = P_T (\tan \varphi_{in} - \tan \varphi_{final}) = 6483,78 (0,6666 - 0,32868) = 2191,3613 \text{ VAR}$$

$$\frac{Q_c}{3} = U_{an}^2 \cdot w \cdot C_\lambda \Rightarrow C_\lambda = \frac{Q_c}{3 \cdot U_{an}^2 \cdot w} = \frac{Q_c}{3 \cdot 2\pi \cdot f \cdot U_{an}^2}$$

$$C_\lambda = \frac{2191,3613}{3 \cdot 2\pi \cdot 50 \cdot 216,3961^2} = 4,96528 \cdot 10^{-5} \text{ F} = 49,6528 \mu\text{F}$$

d) Por ser un sistema equilibrado la $\bar{U}_{N'n} = 0$.

Justificación:

a) line observa el equivalente monophasico la $\bar{U}_n = \bar{U}_{n'n}$

b) $240 \angle 0^\circ - \bar{I}_a \cdot (0,15 + j2,63 + 15 + j10) = 0$

Total (15')

a) ¿P y Q? en las resistencias en función de u . (4')

$$P_{R_1} = \left(\frac{u}{10}\right)^2 \cdot \frac{1}{5} = \frac{u^2}{500} \text{ W} \quad Q_{R_1} = 0$$

$$P_{R_2} = \frac{u^2}{400} \cdot \frac{1}{10} = \frac{u^2}{4000} \text{ W} \quad Q_{R_2} = 0$$

$$P_{R_3} = \frac{u^2}{225} \cdot \frac{1}{2} = \frac{u^2}{450} \text{ W} \quad Q_{R_3} = 0$$

b)
$$\frac{1}{T} = \frac{u}{10^2 \cdot 9} + \frac{u}{20^2 \cdot 10} + \frac{u}{15^2 \cdot 2} = \quad (4')$$

$$90 = \frac{u}{900} + \frac{u}{4000} + \frac{u}{450}$$

$$90 = u \left(\frac{1}{900} + \frac{1}{4000} + \frac{1}{450} \right) = u \cdot (4'47222 \cdot 10^{-3})$$

$$u = 11180'1242 \text{ V.}$$

c) $E = c \cdot (E_{Rcc} \cos \varphi + E_{Xcc} \sin \varphi)$
 \rightarrow carga reactiva (10')

$$c = \frac{P_{2/cos \varphi}}{S_{AT}} = \frac{31248'8}{100.000} = 0'31248$$

$$E_{Rcc} = \frac{50 \cdot 0'8944}{11180'124} \cdot 100 = 0'4$$

$$\cos \varphi_{cc} = \frac{400}{\frac{50}{90} \cdot 8'9444} = 0'8944$$

$$I_{cc} = 8'9424 \text{ A.}$$

$$U_{cc} = 50 \text{ V.}$$

$$E = 0'31248 \cdot (0'4 \cdot 1) = 0'12499 \%$$

$$U_2 = 559'006 - 0'6987 = 558'301 \text{ V}$$